Question Paper of Engineering Service Examination 2010 Electronics and Telecommunication Engineering Paper-II

Objective

1. Consider the following statements:

When compared with a bridge rectifier, a centre-tapped full wave rectifier:

- 1. Has larger transformer utilization factor.
- 2. Can be used for floating output terminals i.e. no input terminal is grounded.
- 3. Needs two diodes instead of four.
- 4. Needs diodes of a lower PIV rating.

Which of the above statements are correct?

(a) 1 and 2 only

(b) 1, 2, 3 and 4

(c) 3 only

- (d) 3 and 4 only
- 2. A linear time-invariant system initially at rest, when subjected to a unitstep input, gives a response $y |t| = te^{-t}$, t > 0. The transfer function of the system is:
 - (a) $\frac{1}{(s+1)^2}$

(b) $\frac{1}{s(s+1)^2}$

(c) $\frac{s}{(s+1)^2}$

- (d) $\frac{1}{s+1}$
- 3. The hexadecimal representation of 657_8 is:
 - (a) 1AFH

(b) D78H


(c) D71H

4.

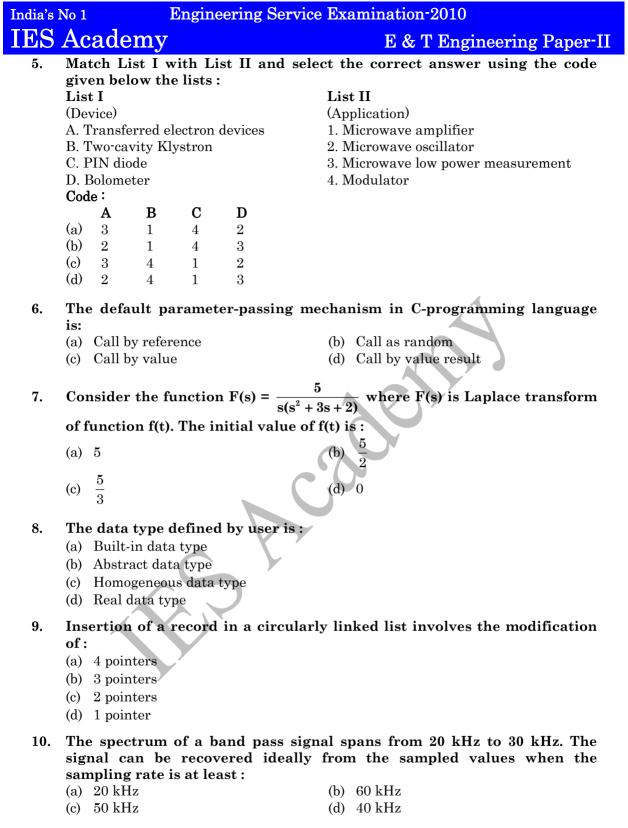(d) 32FH

A 13 bit PCM system performance is better than an 8 bit PCM system

- because:
 - (a) Noise is lower and is proportional to reciprocal of bandwidth
 - (b) Bandwidth is larger and detection is easier
 - (c) Quantization noise is lesser other things being equal
 - (d) Quantization noise is nearly zero since 2¹³ levels are available



A. Rectangular waveguide

1. Plane of polarization

B. Waveguide twists 2. Waveguide tuner

C

IES Academy

E & T Engineering Paper-II


- C. Slotted section
 - ection 3. TE₁₀ mode

D

D. Stub screws

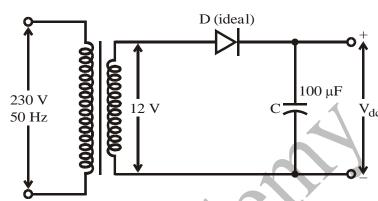4. VSWR measurements

- Code:
- **A B** (a) 2 4
 - (a) 2 4 1 3 (b) 3 4 1 2
 - (c) 3 4 1 2 (c) 2 1 4 3
- (d) 3 1 4 2
- 12.



The output $V_{\rm dc}$ from the above circuit is:

- (a) $12\sqrt{2}$
 - (c) $\frac{24}{}$

- (b) π
 - (d) $\frac{12}{\sqrt{2}}$
- 13. Which of the following data structure is used by a compiler to manage information about variables and their attributes?
 - (a) Abstract syntax tree
 - (b) Linked list
 - (c) Parse table
 - (d) Symbol table
- 14. A transistor works in three regions :
 - 1. Cut-off
 - 2. Active
 - 3. Saturation

While used as switch in digital logic gates, the regions it works in are:

(a) 1 and 2 only

(b) 2 and 3 only

(c) 1 and 3 only

- (d) 1, 2 and 3
- 15. The number of edges in a regular graph of degree D and N vertices is equal to:
 - (a) ND


(b) $\frac{NI}{2}$

(c) N + D

- (d) N^D
- 16. The Boolean expression

India's		eering Service Ex	amination-2010
IES	Academy		E & T Engineering Paper-II
	(a) A (c) C	(b) (d)	B A + B + C
17.	A single bus structur (a) Main frames (b) Mini and micro con (c) Super computers (d) High performance in	nputers	d in :
18.			th G(s) = $\frac{4}{s^2 + 0.4s}$ when subjected system response should be settled
	within 2% tolerance l (a) 1 sec (c) 10 sec	(b)	2 sec 20 sec
19.	The ability to halt the send information on (a) Cycle stealing (c) Polling	buses is called:	y and use this interval of time to Vectoring an interrupt Direct memory access
20.		requency, has rip y equal to 81·2%. dge) rectifier orrect?	mental ripple frequency equal to ople factor of 0.482 and power 2 only 1, 2 and 3
21.	Consider the following 1. Compilers 2. Design 3. Evaluation 4. Instruction set architecture to design (a) 1, 2 and 3 (c) 2, 3 and 4	nitecture included in the n a full computer s (b)	present definition of computer ystem? 1, 3 and 4 1, 2, 3 and 4
22.	The Nyquist rate for (a) 7 kHz (c) 14 kHz	(b)	cos (2000 πt), cos (5000 πt) is : 5 kHz 10 kHz
23.		memory access times the at least: (b)	s 1200 ns and Cache access time is ne is not to exceed 120 ns. The hit 98% 75%
		E mail: icoccador	W@wshan com Page /

24.

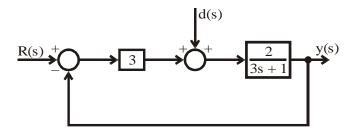

The transfer function from d(s) to y(s). is:

(a) $\frac{2}{3s+7}$

(b) $\frac{2}{3s+1}$


(c) $\frac{6}{3s+7}$

(d) $\frac{2}{3s+6}$

25. An $\frac{I}{O}$ processor controls the flow of information between:

- (a) Cache memory and $\frac{1}{O}$ devices
- (b) Main memory and $\frac{I}{O}$ devices
- (c) Two $\frac{1}{0}$ devices
- (d) Cache and main memory

26.

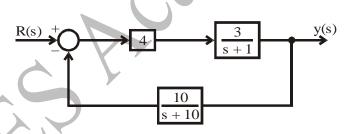

The characteristic equation of the above closed-loop system is:

- (a) $s^2 + 11s + 10 = 0$
 - (b) $s^2 + 11s + 130 = 0$
- (c) $s^2 + 10s + 120 = 0$
- (d) $s^2 + 10s + 12 = 0$

27. The standard SOP expression for Boolean expression $A\bar{B} + AC + BC$ is:

- (a) $A\overline{B}C + \overline{A}BC + A\overline{B}C + ABC$
- (b) $AB\overline{C} + \overline{A}BC + ABC$
- (c) $A\overline{B}C + AB\overline{C} + ABC$
- (d) $\overline{ABC} + AB\overline{C} + A\overline{BC}$

28. The complement of the expression $Y = ABC + AB\overline{C} + \overline{ABC} + \overline{ABC}$ is:

(a) $(A + \overline{B})(A + \overline{C})$

(b) $(\bar{A} + B)(A + C)$

(c) $(A + \overline{B})(\overline{A} + C)$

(d) $(\overline{A} + \overline{B})(A + \overline{C})$

Page 5

India's	s No 1 Engineering Service Examination-2010				
IES	Academy E & T Engineering Paper-II				
29.	Which one of the following has the shortest access time? (a) NMOS EPROM (b) NMOS RAM (c) CNOS RAM (d) Bipolar static RAM				
30.	The main disadvantage of using coaxial cable for microwave signals is its: (a) Low selectivity (b) Low distortion (c) High attenuation (d) High sensitivity				
31.	If the gain of the system is reduced to zero value, the roots of the system in the s-plane: (a) Coincide with zeros (b) Move away from the zeros (c) Move away from the poles (d) Coincide with the poles				
32.	The figure of merit of a logic family is given by the product of: (a) Gain and bandwidth (b) Propagation delay time and power dissipation (c) Fan-out and propagation delay time (d) Noise margin and power dissipation				
33.	In NOR-NOR configuration, the minimum number of NOR gates needed to implement the switching function $X + X\overline{Y} + X\overline{Y}Z$ is: (a) 5 (b) 3 (c) 2 (d) 0				
34.	The addition of open loop zero pulls the root-loci towards: (a) The left and therefore system becomes more stable (b) The right and therefore system becomes unstable (c) Imaginary axis and therefore system becomes marginally stable (d) The left and therefore system becomes unstable				
35.	Match List I with List II and select the correct answer using the code given below the lists: List I A. HTL B. CMOS C. I ² L J. High fan-out J. High est speed of operation J. High noise immunity J. ECL List II List II				
	A B C D (a) 3 4 1 2 (b) 2 1 4 3 (c) 3 1 4 2 (d) 2 4 1 3				
36.	On receiving an interrupt from an $\frac{I}{O}$, device, the CPU:				
	(a) Halts for a predetermined time.(b) Branches off to the interrupt service routine after completion of the current instruction				
	(c) Branches off to the interrupt service routine immediately(d) Hands over control of address bus and data bus to the interrupting device				
www.ie	esacademy.com E-mail: iesacademy@yahoo.com Page 6				
	25, 1 st Floor, Jia Sarai, Near IIT. New Delhi-16 Ph: 011-26537570, 9810958290				

E & T Engineering Paper-II

- Consider the following statements with regard to a PLL:
 - The 'capture range' of a PLL primarily depends upon the slope of transition band edge of the low-pass filter.
 - 2. The 'lock range' is not affected by the slope of transition band of the low-pass filter.

Which of the above statements is/are correct?

- (a) Both 1 and 2
- (d) Neither 1 nor 2 (c) 2 only
- In microprocessor based systems DMA facility is required to increase the speed of data transfer between the:
 - (a) Microprocessor and the I/O devices
 - (b) Microprocessor and the memory
 - (c) Memory and the I/O devices (d) Memory and the reliability system
- If x(t) is of finite duration and is absolutely integrable, then the 'region of 39. convergence' is:
 - (a) Entire s plane
 - (b) From $\sigma = -1$ to $\sigma = +\infty$
 - (c) From $\sigma = +1$ to $\sigma = -\infty$
 - (d) Entire right half plane
- **40.** The quantization noise of a PCM system depends on:
 - (a) Number of quantization levels
 - (b) Step-size
 - (c) Both step-size and number of quantization levels
 - (d) Sampling rate
- Match List I with List II and select the correct answer using the code 41. given below the lists: List II

List I

A. Pipelined ALU

1. RISC


B. Simpler compiler 2. CISC

- C. Separate data and instruction caches 3. Mixed RISC-CISC
 - D. Lesser cycles per instruction

Code:

Ou	~			
	Α	$\mathbf{B}^{\prime\prime}$	\mathbf{C}	D
(a)	3	2	3	1
(b)	1	2	3	3
(c)	3	3	2	1
(d)	3	3	3	1

42.

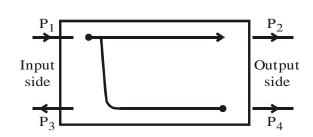

E & T Engineering Paper-II

For the above directional coupler a coupling factor in dB is:

(a) $10 \log_{10} \frac{P_1}{P_4}$


(b) $10 \log_{10} \frac{1}{1}$

(c) $10 \log_{10} \frac{P_2}{P_4}$

(d) $10 \log_{10} \frac{P_1}{P_3}$

43.

India's No 1

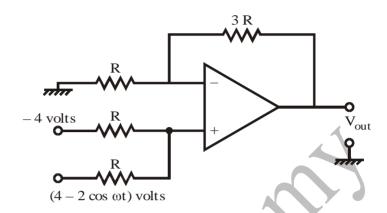

The output of the above OP-amp circuit is:

(a) -0.75 volts

(b) $-2\cos\omega t$ volts

(c) $-8\cos\omega t$ volts

- (d) 16 volts
- 44. A TDM system is to be designed to multiplex the following two signals: $Y_t = 5 \cos(2000 \pi t)$

 $X_1 = 5 \cos (2000 \pi t)$ $X_2 = 2 \cos (2000 \pi t) \cos (3000 \pi t)$

The minimum sampling rate is:

(a) 4 kHz

(b) 5 kHz

(c) 10 kHz

- (d) 6 kHz
- 45. An example of a spooled device is:
 - (a) A graphical display device
 - (b) A line printer used to print the output of a number of jobs
 - (c) A secondary storage devices in a virtual memory system
 - (d) A terminal used to enter input data to a running program
- 46. Which one of the following is a Dirichlet condition?
 - (a) $\int_{t}^{\infty} |x(t)| < \infty$
 - (b) Signal x(t) must have a finite number of maxima and minima in the expansion interval
 - (c) x(t) can have an infinite number of finite discontinuities in the expansion interval
 - (d) x^2 (t) must be absolutely summable
- 47. Consider the following instructions of 8085 microprocessor:
 - 1. MOV B, C
 - 2. STA address
 - 3. ORI byte

The correct sequence in the decreasing order of their respective memory space requirement is:

(a) 3, 2 and 1

(b) 1, 3 and 2

E & T Engineering Paper-II

(c) 1, 2 and 3

- (d) 2, 3 and 1
- 48. A $\frac{D}{A}$ converter has 5 V full-scale output voltage and an accuracy of $\pm 0.2\%$.


The maximum error for any output voltage will be:

(a) 5 mV

(b) 10 m

(c) 20 mV

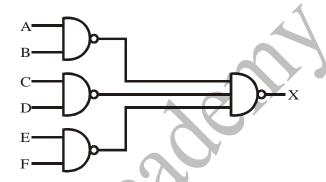- (d) 1·0 mV
- 49. If the CALL instructions of 8085 in the main program is conditional then RETURN instruction in the subroutine can be:
 - (a) Conditional
 - (b) Conditional or unconditional
 - (c) Can be determined by LDA instruction
 - (d) Unconditional
- **50**.



The output X of the above logic circuit is:

- (a) AB + CD + EF
- (b) $\overline{AB} + \overline{CD} + \overline{EF}$
- (c) $(A + B) \cdot (C + D) \cdot (E + F)$
- (d) $(\overline{A+B}) \cdot (\overline{C+D}) \cdot (\overline{E+F})$
- 51. The 'Double minimum' or the "width of minimum power" method is used in microwave measurements for the measurement of:
 - (a) Velocity modulation

(b) Frequency distortion

(c) High V.S.W.R.

- (d) Low V.S.W.R.
- 52. Consider the following statements:
 - 1. The lock range of a PLL is the difference between the highest and lowest frequencies that the PLL can remain in lock onto.
 - 2. The capture range of a PLL is the range of frequencies that the voltage controlled oscillator of a PLL can produce.
 - 3. PLL can be used to synchronize the horizontal and vertical oscillators of TV receivers to incoming sync pulses.

Which of the above statements is/are correct?


(a) 1 only

(b) 3 only

(c) 1 and 3 only

(d) 1, 2 and 3

53.

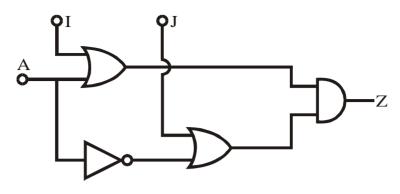


The circuit shown above is to be used to implement the function Z = f(A,B) = \overline{A} + B. The values of I and J are:

- (a) I = 0 and J = B
- (c) I = B and J = 1

- (b) I = 1 and J = B(d) I = B and J = 0
- In the Bode plot of a unity feedback control system, the value of phase **54**. angle of G (jw) is -90° at the gain cross over frequency of the Bode plot, the phase margin of the system is:
 - (a) -180° (c) -90°

- (b) $+ 180^{\circ}$
- + 90° (d)

55.

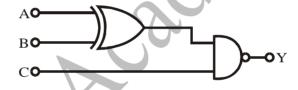

The Boolean expression for the output of the above logic circuit is:

(a) $Y = \overline{AB} + AB + \overline{C}$

(b) $Y = \overline{A}B + A\overline{B} + \overline{C}$

(c) $Y = A \oplus B + \overline{C}$

- (d) $Y = AB + \overline{C}$
- Match List I with List II and select the correct answer using the code 56. given below the lists:

List I

List II

3

1

- A Cavity wave meter
- B. VSWR meter
- C. Bolometer

2

- D. Fraunhofer region
- 1. Impedance measurements
- 2. Frequency measurements
- 3. Antenna measurements
- 4. Microwave power measurements

Code:

	Α	${f B}$	\mathbf{C}	\mathbf{D}
(a)	3	1	4	2
(b)	2	1	4	3
(c)	3	4	1	2

- The Nyquist plot of loop transfer function G(s) H(s) of a closed loop control system passes through the point (-1, j0) in the G(s) H(s) plane. The phase margin of the system is:
 - (a) 0°

(d)

(b) 45°

E & T Engineering Paper-II

(c) 90°


- (d) 180°
- 58. When compared with an RS232C serial port, the USB (Universal Serial Bus):
 - (a) Supports a lower range of peripherals
 - (b) Supports a faster transfer rate
 - (c) Does not support 'Hot plug-ability'
 - (d) Controller in PC can not detect the presence or absence of USB devices
- 59. A ROM is used to store the table for multiplication of two 8-bits unsigned integers. The size of the ROM required is:
 - (a) 256×1

(b) $64k \times 8$

(c) $4k \times 16$


(d) $64k \times 16$


60.

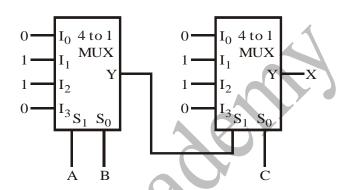

In the above circuit, X is given by:

- (a) $X = A\overline{BC} + \overline{A}B\overline{C} + \overline{ABC} + ABC$
- (b) $X = \overline{A}BC + A\overline{B}C + AB\overline{C} + \overline{ABC}$
- (c) X = AB + BC + AC
- (d) $X = \overline{AB} + \overline{BC} + \overline{AC}$
- 61. Given $X(z) = \frac{1}{1-ax^{-1}}|z| > |a|$ then the region of convergence is (Shaded region):

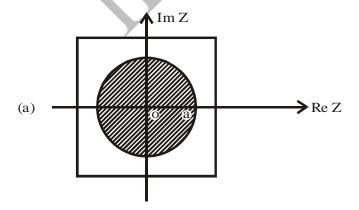

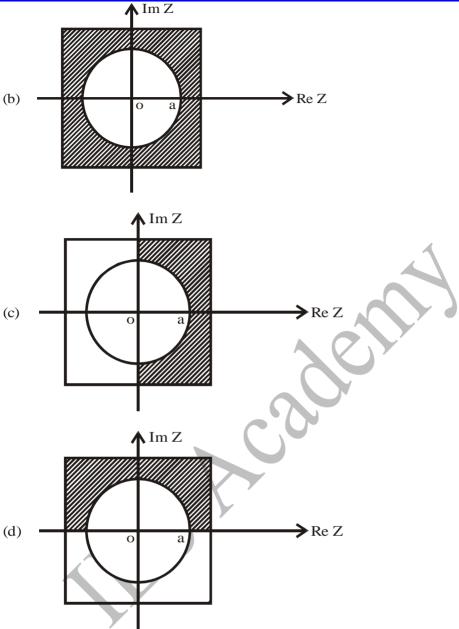


62. A 'DMA' transfer implies :

- (a) Direct transfer of data between memory and accumulator
- (b) Direct transfer of data between memory and $\frac{I}{O}$ devices without the use of μP
- (c) Transfer of data exclusively within μP registers
- (d) A fast transfer of data between μP and $\frac{I}{O}$ devices

E & T Engineering Paper-II

63.

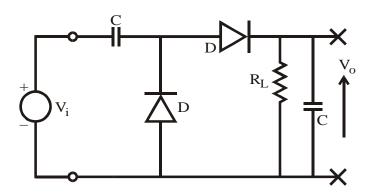


Consider the above circuit, for $V_i = V_m \sin \omega t$, the output voltage V_0 for $R_L \to \infty$ will be:

- (a) Zero
- (c) $2 V_{\rm m}$

- (b) V_m
- (d) $-V_m$

64.

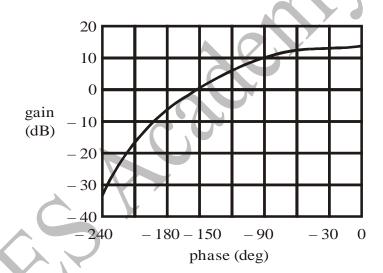

For the Nichols plot shown, the system is:

(a) Unstable

(b) Stable

(c) Overdamped


- (d) Critically stable
- 65. The 8085 has two registers known as primary data pointers. These are registers:
 - (a) B and C

(b) D and E

(c) H and L

- (d) C and D
- 66. The correct statement is:
 - (a) PROM contains a programmable AND array and a fixed OR array
 - (b) PLA contains a fixed AND array and a programmable OR array
 - (c) PROM contains a fixed AND array and a programmable OR array
 - (d) PLA contains a programmable AND array and a fixed OR array

67.

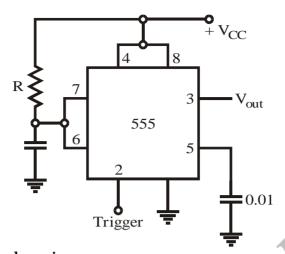

The circuit shown above is a:

- (a) Bi-stable multi-vibrator
- (b) Mono-stable mult-vibrator
 - (c) Free running multi-vibrator
- (d) Ramp generator

68. Consider the following statements:

- A multiplexer is analogous to a rotary switch.
- A decoder is a combinational logic circuit that converts binary information from 'n' input lines to a maximum of 2n distinct elements at the output.
- The Boolean expression for the output different 'D' from a full subtractor is 3. exactly the same as the output sum 'S' from a full adder.

Which of the above statements is/are correct?

(a) 2 and 4 only (c) 1 and 3 only

- (d) 1, 2 and 3
- A ship to ship communication system is affected by fading. A useful 69. solution which can be used is:
 - (a) A more directional antenna
 - (b) A broadband antenna
 - (c) Use of frequency diversity

 - (d) Use of space diversity
- **70.** The impulse response h[n] of an LTI system is h[n] = u[n + 3] | u[n - 2] - 2u[n - 7].

Then the system is:

- 1. Stable
- 2. Casual
- Unstable 3.
- 4. Not causal.
- Which of these are correct?
- (a) 1 and 2 only

(b) 2 and 3 only


3 and 4 only

- (d) 1 and 4 only
- 71. For the experimental study of small microwave antennas, a free space environment with minimum interference by external objects, the facilities required are:
 - (a) RF screens, VSWR meter, waveguide twist

E & T Engineering Paper-II

- (b) UHF screens, slotted waveguides, power meter
- (c) Anechoic chamber, Network analyzer, Pattern recorder
- (d) Dark room facility, Digital recorder, Bolometer
- 72. READY signal in 8085 is useful when the CPU communicates with:
 - (a) A slow peripheral device
- (b) A fast peripheral device
- (c) A DMA controller chip
- (d) A PPl chip

73.

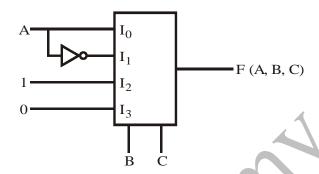

A 4×1 MUX is used to implement a 3-input Boolean function is as shown above. The Boolean function F(A, B, C) implemented is:

- (a) $F(A, B, C) = \Sigma (1, 2, 4, 6)$
- (b) $F(A, B, C) = \Sigma (1, 2, 6)$
- (c) $F(A, B, C) = \Sigma(2, 4, 5, 6)$
- (d) $F(A,B,C) = \Sigma (1, 5, 6)$
- 74. Population inversion in semiconductor laser diode is achieved by:
 - (a) Lightly doping p and n sides
 - (b) Introducing trap centres on p and n sides
 - (c) Heavily doping p and n sides
 - (d) Reverse biasing the junction

75. In the following 8085 program how many times (decimal) is the DCRC executed?

LOOP: MVIC, 78 H

DCRC

JNZ LOOP

HLT


(a) 119

(b) 120


(c) 78


- (d) 77
- 76. Processing of MOS ICs is less expensive than bipolar IC_s primarily because they:
 - (a) Use cheaper components
 - (b) Need no component isolation
 - (c) Require much less diffusion steps
 - (d) Have very high packing denisty


77.

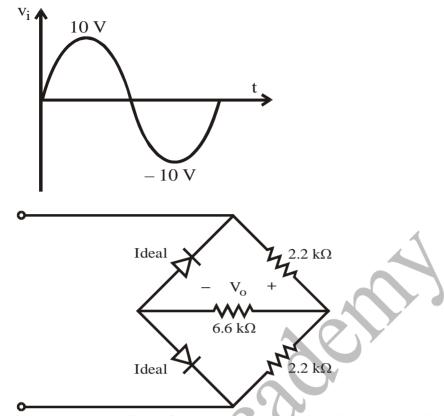

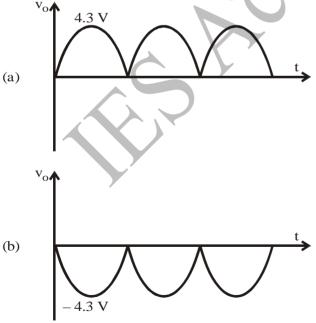
The correct waveform for output (V_o) for the above network is :



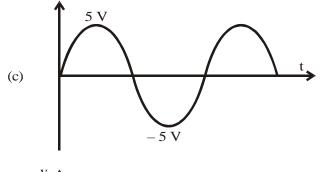

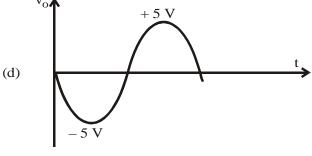

78.

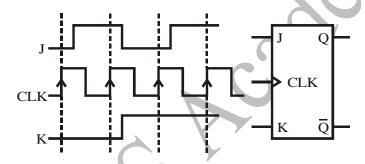

The J-K flip-flop shown above is initially reset, so that Q=0. If sequence of four clock pulses is then applied, with the J and K inputs as given in the figure, the resulting sequence of values that appear at the output Q starting with its initial state, is given by:

(a) 01011

(b) 01010

(c) 00110

(d) 00101

- 79. A single instruction to clear the lower four bits of the accumulator in 8085 assembly language is:
 - (a) XRl 0FH

(b) ANl F0H

(c) XRl F0H

(d) ANI 0FH

E & T Engineering Paper-II

80.

X	Y	Q_{n+1}
0	0	1
0	1	Q _n
1	0	\bar{Q}_n 1
1	1	0

An X-Y flip flop, whose characteristic table is given above is to be implemented using J-K flip flop. This can be done by making:

(a) $J = X, K = \overline{Y}$

(b) $J = \overline{X}$, K = Y

(c) $J = Y, K = \overline{X}$

- (d) $J = \overline{Y}, K = X$
- The Z-transform of -u (-n-1) is: 81.
 - (a) $\frac{Z}{Z-1}$ with |Z| > 1

(b) $\frac{Z}{Z-1}$ with 0 < |Z| < 1(d) $\frac{Z}{Z-1}$ with |Z| = 0

(c) $\frac{Z}{Z-1}$ with |Z| = 1


- 82. The interface chip used for data transmission between 8086 and a 16 bit
 - ADC is:
 - (a) 8251

(b) 8253

(c) 8255

(d) 8259

83.

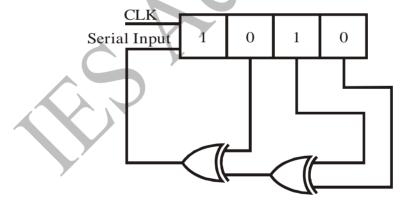

The shift register shown in the given figure is initially loaded with the bit pattern 1010. Subsequently the shift register is clocked, and with each clock pulse the pattern gets shifted by one bit position to the right. With each shift, the bit at the serial input is pushed to the msb position. After how many clock pulses will the content of the shift register become 1010 again?

(a) 3

(b) 7

(c) 11

(d) 15


India's No 1

IES Academy

E & T Engineering Paper-II

- 84. A microprocessor based system can perform many different functions, because:
 - (a) Its operation is controlled by software
 - (b) It is digital system
 - (c) It uses a RAM
 - (d) It can be controlled by input and output devices

85.

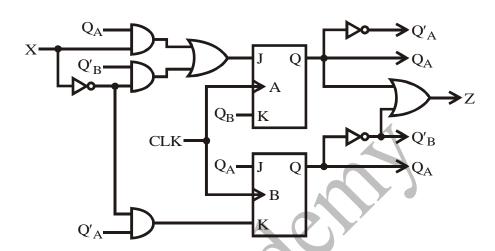

Analyze the sequential circuit shown above in figure. Assuming that initial state is 00, determine what input sequence would lead to state 11?

(a) 1-1

(b) 1 - 0

(c) 0 - 0

- (d) State 11 is unreachable
- 86. Which of the following instructions copies a byte of data into the accumulator from the memory address given in the instruction?
 - (a) LDA address


B


- (b) LDAX
- (c) LHLD address
- (d) STA address
- 87. The magnitude and phase of the transfer function $G(s) = \frac{1}{s+1}$ at $\omega = 1$ is:
 - (a) 0.707 and 45°
 - (b) -3 dB and 0.78 rad
 - (c) $0.707 \text{ and } -45^{\circ}$
 - (d) $3 dB and 90^{\circ}$
- 88. In a typical satellite communication system, which of the following could be the up-link and down-link frequencies respectively?
 - (a) 40 GHz and 60 GHz
- (b) 60 GHz and 40 GHz


(c) 6 GHz and 4 GHz


(d) 4 GHz and 6 GHz

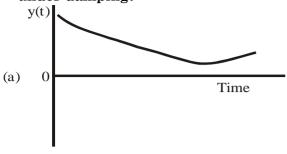89. Which of the following is the response of a spring-mass-damper with under-damping?



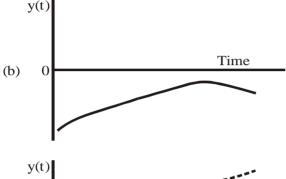

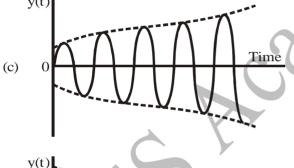


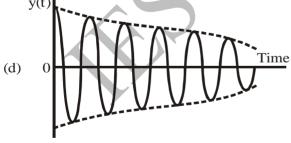

- 90. The output data lines of microprocessors and memories are usually tristated, because:
 - (a) More than one device can transmit information over the data bus by enabling only one device at a time.
 - (b) More than one device can transmit information over the data bus at the same time
 - (c) The data lines can be multiplexed for both input and output
 - (d) It increases the speed of data transfers over the data bus

E & T Engineering Paper-II

91.

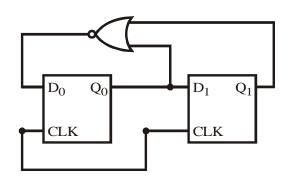


For the circuit shown, the counter state (Q1, Q0) follows the sequence :

- (a) 00, 01, 10, 11, 00
- (b) 00, 01, 10, 00, 01
- (c) 00, 01, 11, 00, 01
- (d) 00, 10, 11, 00, 10
- 92. From the point of view of stability and response speed of a closed loop system, the appropriate range for the value of damping ratio lies between:
 - (a) 0 to 0.2
 - (c) 0.8 to 1.0

- (b) 0.4 to 0.7
- (d) 1·1 to 1·5

93.

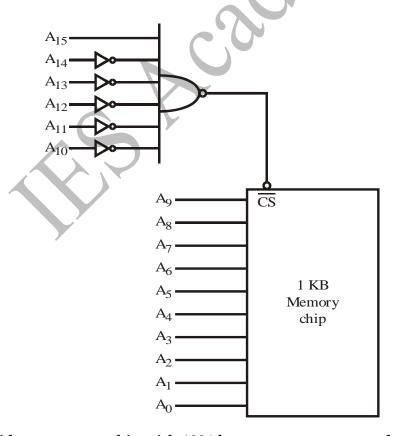

Consider a memory chip with 1024 bytes storage connected to a 8085 chip address lines (or any microprocessor with 16 address lines) as above. What is the range of memory address?


Page 21

E & T Engineering Paper-II

- (a) 0000 H to 03 FFH
- (c) F000 H to F3FFH

- (b) 1000 H TO 13 FFH
- (d) 0000 H to FFFFH
- 94. The output stage of a transponder onboard a satellite has a maximum power output of 10 watts. However, it is not operated at the maximum power output in order to:
 - (a) Conserve the available limited battery power
 - (b) Reduce noise due to devices
 - (c) Avoid intermodulation distortion
 - (d) Avoid heating up of the satellite beyond a pre set value
- 95. The purpose of a start bit in RS232 serial communication protocol is:
 - (a) To synchronize receiver for receiving every byte
 - (b) To synchronize receiver for receiving a sequence of bytes
 - (c) As a parity bit
 - (d) To synchronize receiver for receiving the last byte

96.

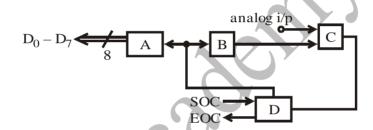

Consider the above block diagram of a successive approximation $\frac{A}{I}$

converter. Match List I with List II and select the correct answer using the code given below the lists:

List I	
(Block)	

List II (Name)

À.

1. Comparator

В.

2. $\frac{A}{D}$ converter

 α

D

C.

3. Successive approximations register

D.

4. Output port

Code:

- A B C D
 (a) 4 1 2 3
- (a) 4 1 2 (b) 3 1 2
- (b) 3 1 2 4 (c) 4 2 1 3
- (d) 3 2 1
- 97. The transfer function $G(s) = \frac{10}{(3s+1)}$ has a corner frequency at:
 - (a) 3 rad /s


(b) 0.33 rad /s

(c) 1 rad /s

(d) 30 rad/s

- 98. A 10 bit $\frac{A}{D}$ converter is used to digitize an analog signal in the 0 to 5 V range. The maximum peak to peak ripple voltage that can be allowed in the DC supply voltage is, nearly:
 - (a) 100 mV (c) 25 mV

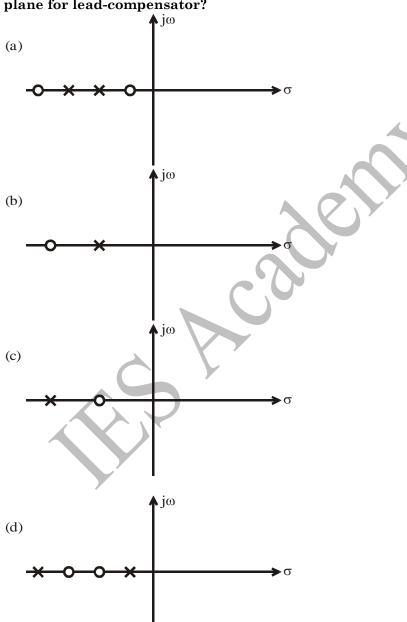- (b) 50 mV (d) 5:0 mV
- 99. Which one of the following represents the pole-zero location in the splane for lead-compensator?



- 100. Consider the following application:
 - 1. Wind tunnel simulation
 - 2. Real-time video viewing

A computer is used for:

Engineering Service Examination-2010

IES Academy

E & T Engineering Paper-II

(a) Neither 1 nor 2

(b) Both 1 and 2

(c) 1 only

(d) 2 only

Directions :-

India's No 1

Each of the next Twenty (20) items consists of two statements, one labelled as the 'Assertion (A)' and the other as 'Reason (R)'. You are to examine these two statements carefully and select the answers to these items using the codes given below:

Codes:

- (a) Both A and R are individually true and R is the correct explanation of A
- (b) Both A and R are individually true but R is not the correct explanation of A
- (c) A is true but R is false
- (d) A is false but R is true
- **101. Assertion (A):** The TTL NAND gate in tristate output configuration can be used for a bus arrangement with more than one gate output connected to a common line

Reason (R): The tristate configuration has a control input, which can detach a logic level $\left(\frac{0}{1}\right)$ from coming onto the bus line.

 $\textbf{102. Assertion (A):} \\ \textbf{Integral windup effect in controller causes excessive overshoot.}$

Reason (R): Presence of saturation in controller and actuator deteriorates the PID control.

- 103. Assertion (A): Steady state error can be reduced by increasing integral gain.

 Reason (R): Overshoot can be reduced by increasing derivative gain.
- **104.** Assertion (A): Source produces two symbols A and B with probability $\frac{3}{4}$ and $\frac{1}{4}$ respectively. For error free transmission this source should be cooled using Shannon-Fano code.

Reason (R): For better transmission efficiency, source and channel must be matched.

105. Assertion (A): Frequency modulation and phase modulation both produce different set of frequency bands for the same modulation depth.

 ${f Reason}$ (R): Frequency modulation and phase modulation vary the carrier phase angle or its rate.

106. Assertion (A): In amplitude modulation systems the value of modulation index should be around 1.

 $Reason\ (R)$: The power carried in the intelligence carrying sidebands increases with the modulation index.

107. Assertion (A): When coding signals like speech signals a-law or $\mu\text{-law}$ quantizers are used.

Reason (R): A-law and μ -law quantizers occupy smaller bandwidth than uniform quantizers.

108. Assertion (A) : PCM / FM systems transmit PCM pulses by modulating a high frequency carrier and hence occupy large band width and eliminate distortion.

India's No 1 Engineering Service Examination-2010

IES Academy

E & T Engineering Paper-II

Reason (R): Large bandwidth ensures SNR tide off and hence distortionless transmission is ensured.

- 109. Assertion (A): It is not necessary to incorporate a very low noise amplifier in a communication satellite.

 Pageon (P): The page temperature of the satellite entenns is usually high since
 - **Reason (R):** The noise temperature of the satellite antenna is usually high, since the beam is covered by the earth.
- 110. Assertion (A): A magnetron is not an amplifier, but an oscillator producing microwaves.
 - **Reason (R):** In making their circular passes in the interaction space of a magnetron, the electrons excite the resonant cavities into oscillations.
- 111. Assertion (A): The slow wave wave structure of a TWT is provided with an attenuator.Reason (R): This is done for preventing oscillations in the device.
- 112. Assertion (A): Generally, magnetrons are operated in π modes. Reason (R): Frequency for π mode can be easily separated from adjacent modes.
- 113. Assertion (A): The impedance of a matched load is equal to characteristic impedance of line.
 - Reason (R): A matched termination absorbs the entire power incident on it.
- 114. Assertion (A): In microwave point-to-point communication systems, parabolic reflector antennas are generally used.
 Reason (R): A parabolic reflector antenna receiver has the property of focusing all axial rays to its focus and when used as transmitter with a feed at the focus, it will generate parallel beams along the axis with a pencil beam radiation pattern.
- 115. Assertion (A): A Cassegrain antenna uses a main paraboloidal reflector and a relatively small hyperboloidal sub-reflector with a small horn-feed at the vertex of the main paraboloidal reflector.
 Reason (R): The optical technique developed by William Cassegrain was used in telescope design to obtain large magnification with a physically short telescope. This configuration is found to be effective in the design of microwave antenna also.
- 116. Assertion (A): In microwave communication links, intensive fading at 18 GHz
- band occurs due to rain-drop attenuation.

 Reason (R): Collective scattering from water droplets in the atmosphere will result in diminution of energy in the forward path and this is maximum at the 18 GHz band because the criterion for scattering are more satisfied by the wavelength dimensions at these frequencies.
- 117. Assertion (A): In satellite communication technique, frequency reuse effectively doubles the bandwidth and information capacity of a satellite.
- doubles the bandwidth and information capacity of a satellite. **Reason (R):** Electromagnetic waves radiated from a transmitting antenna could be received by a distant receiving antenna by tuning the receiver in terms of
- 118. Assertion (A): The main difference between a microprocessor and a microcontroller is that the former does not have any on-chip main memory whereas latter has.

Reason (R): A microprocessor does not need memory to run programs.

frequency and polarization.

Engineering Service Examination-2010

IES Academy

India's No 1

E & T Engineering Paper-II

- 119. Assertion (A): Logic analyzer offers a "delayed sweep".

 Reason (R): Because the logic analyzer "sweep" is really a clock signal.
- **120. Assertion (A):** When you turn on your PC, a process called POST (power-on-self-test) begins with an electrical signal.

Reason(R): The electrical signal restores left over data from the chip's internal memory register.

